



(AN UNDERTAKING OF BHAKTAPUR MUNICIPALITY)

KHWOPA COLLEGE OF ENGINEERING
AFFILIATED TO TRIBHUVAN UNIVERSITY

**A
Report on
LAB 3: FIXED CAPACITOR THYRISTOR CONTROLLED
REACTOR**

Submitted By :

Shubhanga Aryal KCE078BEL038

Submitted To:

Er. Sabin Kasula

Lecturer, KhCE

Department of Electrical Engineering

KHWOPA COLLEGE OF ENGINEERING

Libali-08, Bhaktapur

LAB 3

FIXED CAPACITOR THYRISTOR CONTROLLED REACTOR

1 Objectives

To understand the working of a fixed capacitor thyristor controlled reactor(FCTCR) and analyze the waveforms in MATLAB/Simulink.

2 Software Used

- MATLAB/Simulink.

3 Theory

A basic VAR generator using a fixed capacitor with a thyristor controlled reactor is as shown in the Figure 1(a) below:

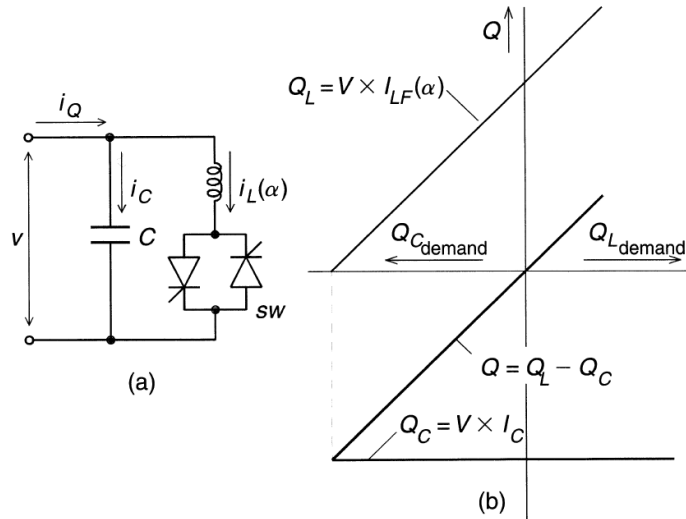


Figure 1: Fixed Capacitor Thyristor Controlled Reactor

The current in the reactor is varied similarly to the thyristor controlled reactor method. The FCTCR may be considered essentially to consist of a variable reactor (controlled by a delay angle α) and a fixed capacitor. The constant capacitive var generation of the fixed capacitor is opposed by the variable var absorption (Q_L) of the thyristor controlled reactor to yield the total var output required as seen in Figure 1(b). At zero var output,

the capacitive and inductive currents become equal and thus the capacitive and inductive vars cancel out. With a further decrease of angle α the inductive current becomes larger than the capacitive current, resulting in a net inductive var output. At zero var output, the capacitive and inductive currents become equal and thus the capacitive and inductive vars cancel out. With a further decrease of angle α the inductive current becomes larger than the capacitive current resulting in a net inductive var output. At zero delay angle, the thyristor controlled reactor conducts current over the full 180° interval, resulting in maximum inductive var output that is equal to the var generated by the capacitor and those absorbed by the fully conducting reactor.

When the inductive load decreases, the fixed capacitor will overcompensate. This overcompensation is neutralized reducing the firing angle of TCR branch with the help of a closed loop control system.

4 Observation

The circuit diagram to simulate the working of FCTCR is as shown in the figure below:

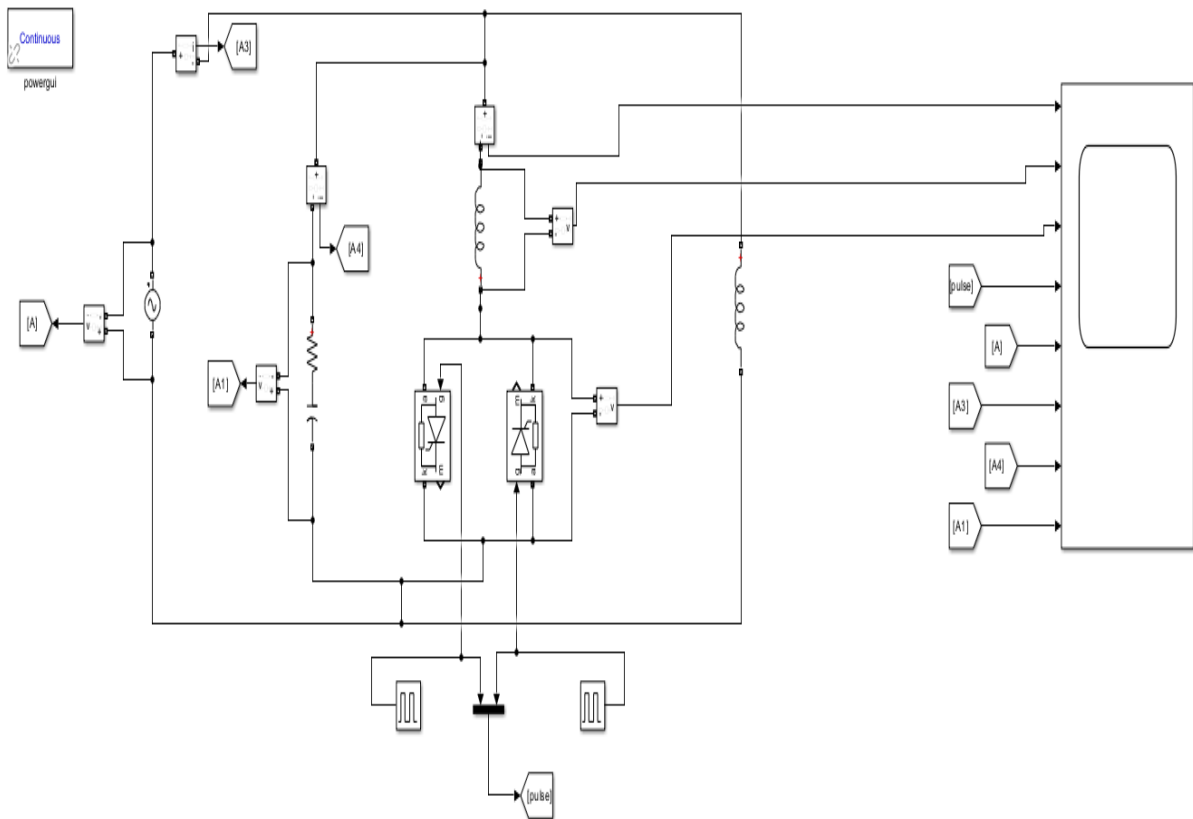


Figure 2: Simulation Model of FCTCR

The observation was taken for $X_c > X_L$ for various firing angles and the value of X_C was $10\text{e-}3(\text{F})$ where as the load inductor was $1\text{e-}3(\text{H})$.

For $\alpha = 90^\circ$:

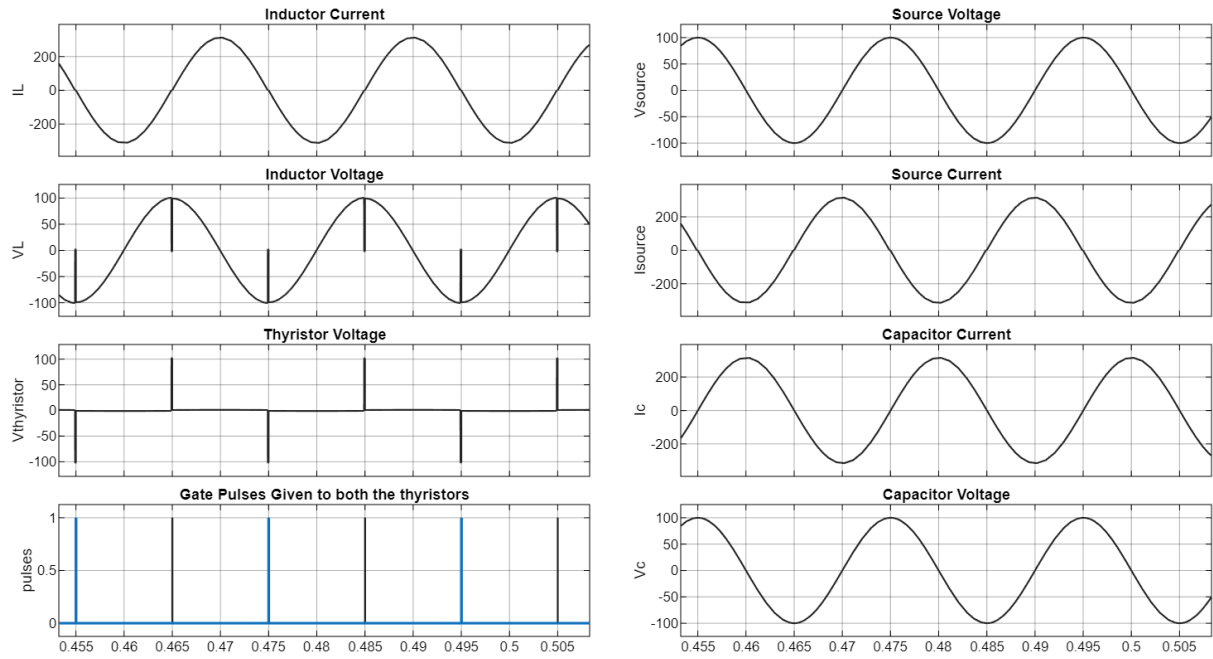


Figure 3: FCTCR Waveforms for $\alpha = 90^\circ$

For $\alpha = 120^\circ$:

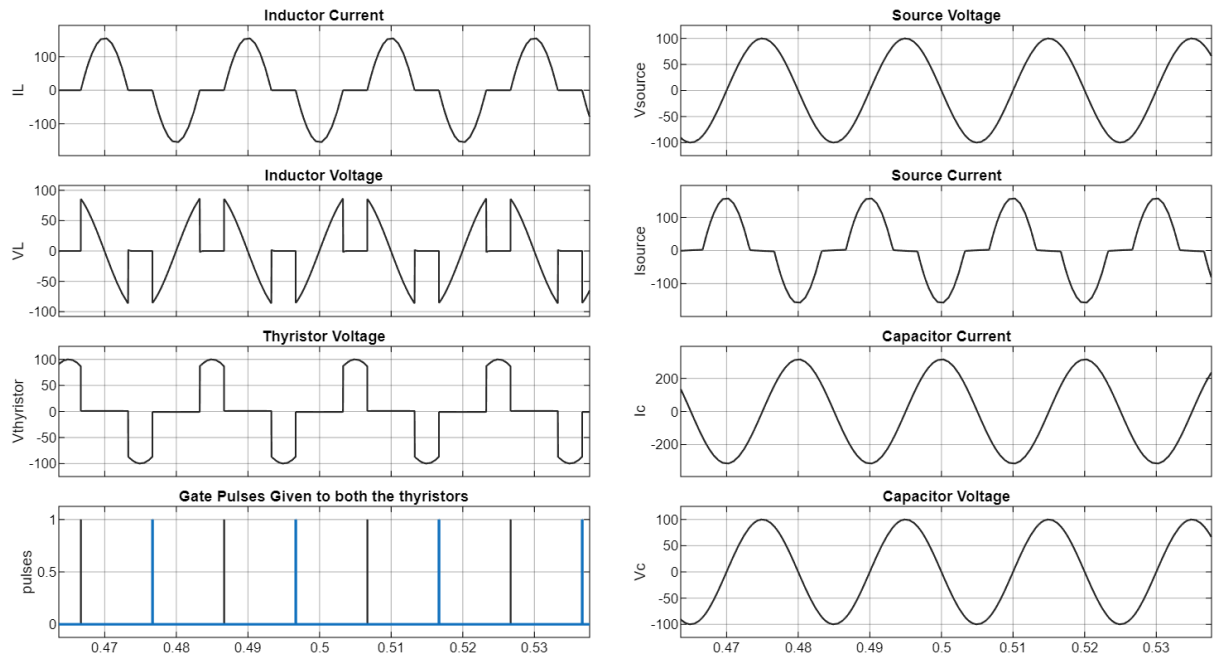


Figure 4: FCTCR Waveforms for $\alpha = 120^\circ$

For $\alpha = 180^\circ$:

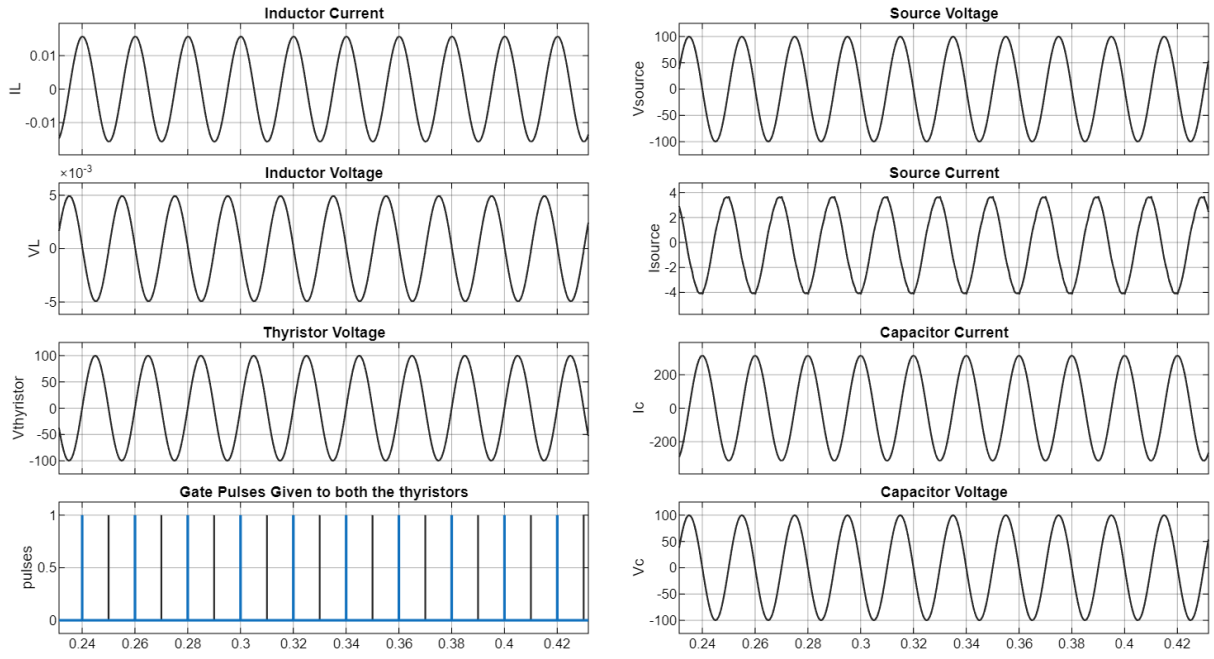


Figure 5: FCTCR Waveforms for $\alpha = 180^\circ$

Same process was repeated for $X_L > X_C$ and observed for the same firing angle as before:

For $\alpha = 90^\circ$:

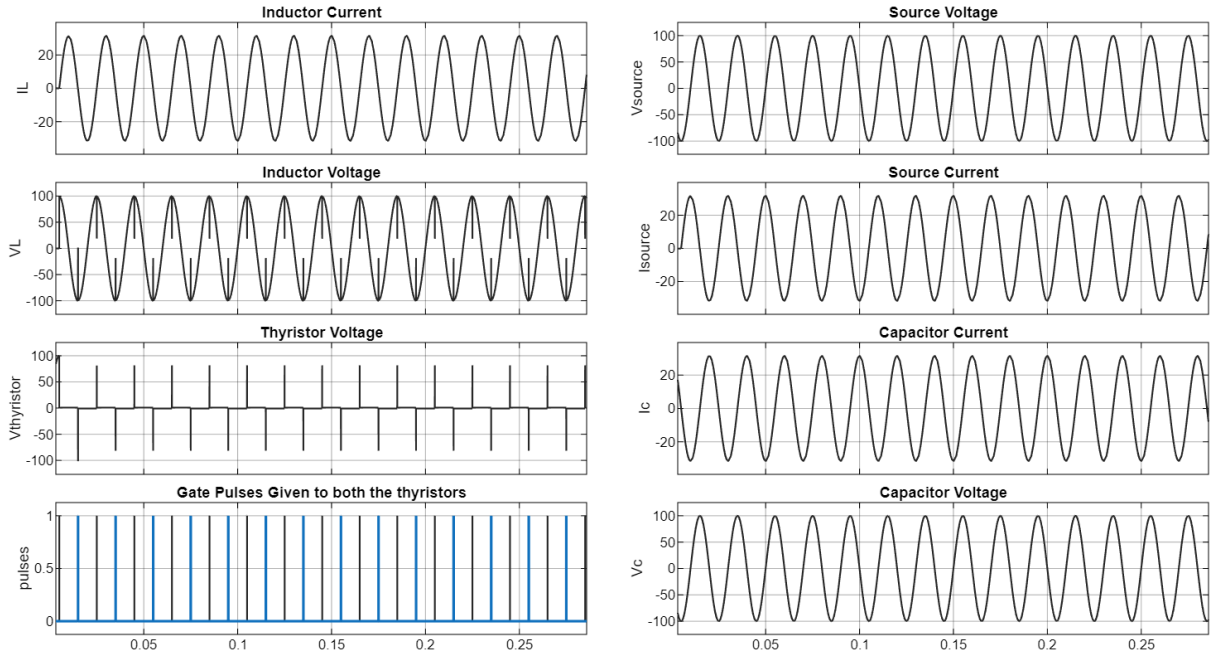


Figure 6: FCTCR Waveforms for $\alpha = 90^\circ$ ($X_L > X_C$)

For $\alpha = 120^\circ$:

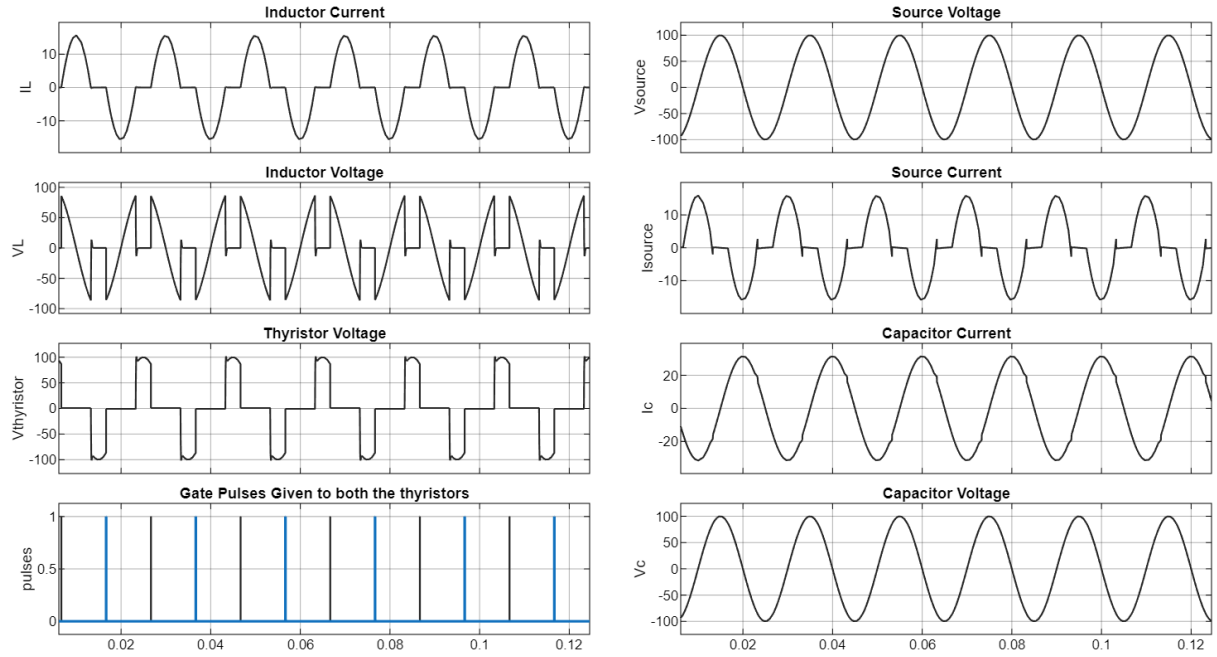


Figure 7: FCTCR Waveforms for $\alpha = 120^\circ$ ($X_L > X_C$)

For $\alpha = 180^\circ$:

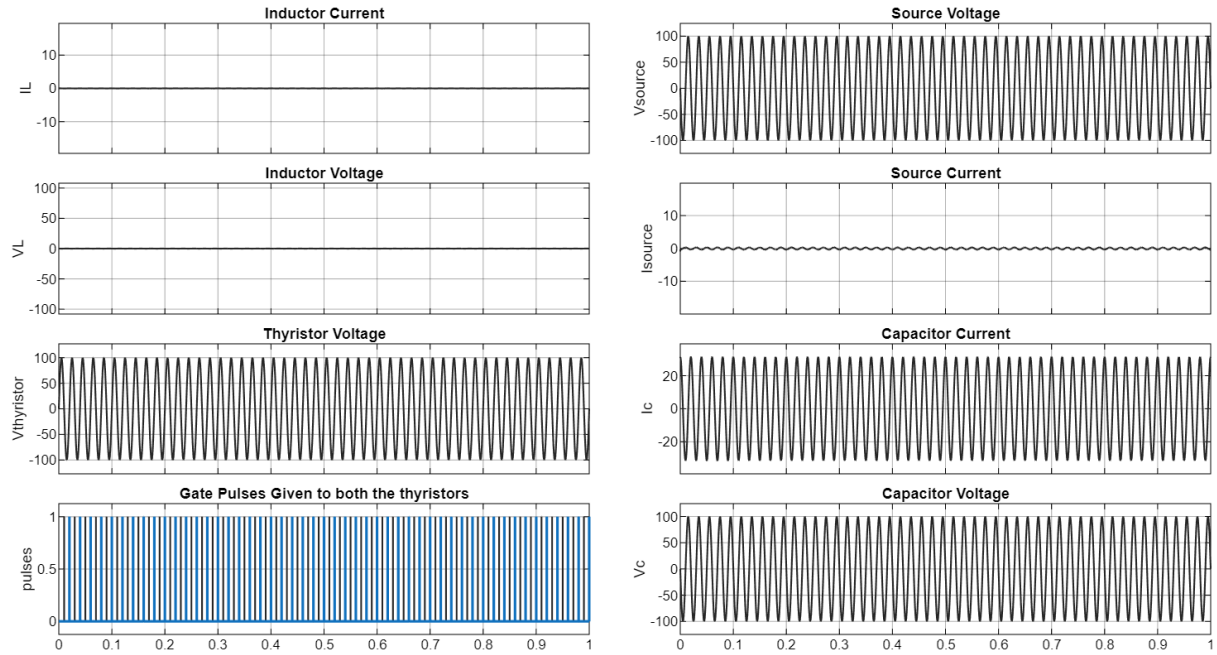


Figure 8: FCTCR Waveforms for $\alpha = 180^\circ$ ($X_L > X_C$)

5 Discussion

In this lab, we simulated the working of fixed capacitor thyristor controlled reactor for various firing angles and two conditions. At $\alpha = 90^\circ$ the thyristor pairs are fully

conducting, and the scheme generated reactive power as shown in the figure. Between 90 and 180, we can see that the inductor current is leading with the source voltage and even at 180 degrees. Hence, we can say that the scheme generates reactive power.

When inductive mode, the source current or the inductive current was greater than the capacitive current. And hence at 90 degrees the compensation current is purely sinusoidal and consumes reactive power. At 120 degrees, we can see that the compensating current is not sinusoidal and is still lagging with the source voltage. Hence, this scheme, consumes reactive power.

However at 180 degrees, the thyristors are completely off and the inductor current and voltage are completely near equal to zero. In this case, in both the scheme it generates reactive power, which matches the theoretical expectation.

6 Conclusion

Thus, the working of FCTCR and its effect on different firing angles was simulated and understood.